

Project

Documentation

Project Title: 3D Led Cube

Team members: Hardik Soni,Saurabh Kataria,Akshay Kumar,Shivam Agarwal

Team mentor: Vinay Kyatham, Anurag Prabhakar.

Basic Aim:

To create a 3D led cube which is capable of showing pre-defined animations.

Integrating it with MATLAB to display graphs.

Motivation:

We searched for some arduino projects on internet there we found about LED cube.We were really impressed to see it.

So, we finally decided to make LED cube.

Theory:

A LED cube is like a LED screen , but it is special as it has

3D. We can think of it as low resolution displays.

In normal displays it is normal to stack pixels closer to each other in order for better resolution but LED cube has its limits.

Working:

The LED cube has 512 LEDs. So it is impractical to dedicate an IO port for each LED. Instead LED cube relies on an optical phenomenon called Persistence of vision. If you flash an LED really fast it will remain in your retina for some time even after the LED is switched off. By flashing each layer of the cube very fast after one another it gives the feeling of 3D.

With this setup we will need only 64 (anode) + 8 (layers) IO ports to control each LED.

Anatomy of LED cube:

LED has two legs, one positive and one negative. The positive end is connected to the pillars of the LED cube which acts as anode. The negative one is connected to the layer.

Hence, to switch on a particular LED we have to give current to the corresponding pillar and ground the layer.

IO Port requirements and multiplexing:

For an 8x8x8 LED cube we need 72 IO pins. But we can reduce this by further multiplexing. We used nine 4051 8-bit multiplexer. 8 multiplexer used to control the pillars and last one used to control the layers. This multiplexer had eight IO pins to control pillars and three pins to control the values assigned to these eight pins.

Power Supply:

This step can be easily overlooked as we think that LEDs draw less current but here there are 512 LEDs so there might be power problem. So, we decided to use Switched-Mode Power Supply (SMPS). It is a source of constant voltage and high current.

Choosing and Testing LEDs:

In this we thought to use diffused LEDs as using clear LEDs might pose some problems like if a particular clear LED is on then its brightness may cause the nearby LEDs which are switched off to appear switched on. So, we used diffused LEDs. Also before using them in cube we tested each LED by making small circuit on breadboard.

Circuit:

We have used 9 multiplexer. The first 8 multiplexer are for the pillars (anode). The 8 IO pins of a multiplexer are connected to base of NPN transistor. The emitter is connected to pillar and collector is given 5V. The 8 IO pins of multiplexer for layers (cathode) is also connected to base of NPN transistor but here the collector is connected to the layers and emitter is grounded.

The 4 pins of multiplexer will be connected to the ARDUINO MEGA. These four pins will decide what value to be assigned to the IO pins. So, we will use 36 pins of arduino. The power source is given by SMPS.

Code:

The software used for coding programmes for the cube is Arduino 1.0.2/1.5.2 and the matlab programs require arduino support package which is downloaded from arduino website.

With Matlab GUI interface we created buttons which when clicked trigger some code which plots a graph and controls the arduino.

Future improvisations:

Variation in size can give better resolution.

Use of Bit Angle Modulation can improve brightness of LEDs.

Full integration with MATLAB to plot 3D interactive graphs.

Use of RGB LEDs.

Important Links:

A demonstration of LED cube

<http://www.youtube.com/watch?v=6mXM-oGggrM>

Guide on making LED cube

<http://www.instructables.com/id/Led-Cube-8x8x8/?ALLSTEPS>

<http://www.hownottoengineer.com/projects/lc.html>

A word of thanks:

First of all we would like to thank the Coordinators of Electronics Club Sonu Agarwal, Swapnil Upadhyay, Shivendu Bhushan to give us an opportunity to make a summer project.

We would also like to thank our mentors Anurag

Prabhakar and Vinay Kyatham who guided our way to complete the project.

At last, It is always fun in learning something new. We learned many things about electrical circuits and some programming tools which may help us in future.